

December 1982

# Using the 2817 Intelligent E<sup>2</sup>PROM

**Justin Orion**  
Applications Engineering  
**Harry Look**  
Product Marketing Engineer  
Non-Volatile Memory Division

Intel Corporation makes no warranty for the use of its products and assumes no responsibility for any errors which may appear in this document nor does it make a commitment to update the information contained herein.

The following are trademarks of Intel Corporation and may only be used to identify Intel Products:

BCP, CREDIT, i, ICE, i<sup>2</sup>-ICE, ICS, iLBX, i<sub>m</sub>, iMMX, Insite, INTEL, intel, Inteleview, Inteltec, intelligent Identifier™, intelligent Programming™, Intellink, iOSP, iPDS, iRMS, iSBC, iSBX, iSXM, Library Manager, MCS, Megachassis, Micromainframe, MULTIBUS, Multichannel™ Plug-A-Bubble, MULTIMODULE, PROMPT, Promware, RMX/80, RUPI, System 2000, and UPI, and the combination of ICE, iCS, iRMX, iSBC, MCS, or UPI and a numerical suffix.

MDS is an ordering code only and is not used as a product name or trademark. MDS® is a registered trademark of Mohawk Data Sciences Corporation.

\* MULTIBUS is a patented Intel bus.

Additional copies of this manual or other Intel literature may be obtained from:

Intel Corporation  
Literature Department  
3065 Bowers Avenue  
Santa Clara, CA 95051

# Using the 2817 Intelligent E<sup>2</sup>PROM

## Contents

A NEW AND REVOLUTIONARY TYPE OF MEMORY .....	1
DESIGNING IN THE 2817 .....	1
SIMPLE INTERFACE REQUIREMENTS .....	1
A WRITE PROTECTION CIRCUIT EXAMPLE .....	2
ADVANTAGE OF STATIC 21V .....	3
21V IS EASY TO OBTAIN .....	3
LARGE ARRAYS .....	3
CONNECTING THE RDY/BUSY OUTPUT TO THE SYSTEM .....	4
FUTURE UPGRADABILITY TO THE 5V-ONLY 2817A .....	5
VENDOR INFORMATION .....	6



## A NEW AND REVOLUTIONARY TYPE OF MEMORY

The Electrically Erasable PROM (E<sup>2</sup>PROM) provides the system designer with an inexpensive, non-volatile, in-circuit alterable memory. The E<sup>2</sup>PROM is superior in reliability to electro-mechanical, non-volatile storage media such as floppy disks. E<sup>2</sup>PROMs can operate in environments of dust particles, vibration, and wide temperature ranges. The E<sup>2</sup>PROM offers additional flexibility over UV EPROMs because of in-circuit alterability.

Unlike the previous 2816 E<sup>2</sup>PROM, the 2817 E<sup>2</sup>PROM has on-chip address/data latches, auto erase-before-write, and  $\overline{\text{RDY}}/\overline{\text{BUSY}}$  (RDY/BUSY) output intelligence. These powerful features, discussed later in more detail, are provided to the user through a high level of on-chip integration.

Applications which include remote firmware updating, user-defined functions, calibration constants, configuration parameters, and data logging are easily implemented with the 2817.

For example, in the field of data communications, 2817 E<sup>2</sup>PROMs are used to store table lookup data that configure the protocol for a given I/O channel. Because the data is stored in E<sup>2</sup>PROM, the user can quickly reconfigure the I/O channel to a different protocol via an end system keyboard. The 2817 E<sup>2</sup>PROMs provide user flexibility as well as user friendly implementation. Transmission errors and service information can also be logged into the E<sup>2</sup>PROM.

In navigation or radar systems, program code is often changed to store new flight information. Prior to E<sup>2</sup>PROMs, the EPROM boards containing the code had to be physically removed to be reprogrammed. With the 2817 E<sup>2</sup>PROM, reprogramming is easily accomplished because of the in-circuit alterability of E<sup>2</sup>PROMs.

The realm of potential applications is limited only by the user's imagination. The 2817 E<sup>2</sup>PROM is already used in an extensive spectrum of applications. E<sup>2</sup>PROMs are used not only to replace other non-volatile storage mediums in current applications but also to make possible new applications.

### DESIGNING IN THE 2817

The 2817 E<sup>2</sup>PROM is easy to use. Reading is accomplished in the same manner as with the 2716 EPROM:  $\overline{\text{CE}} = \overline{\text{OE}} = \text{LOW}$ , and  $\overline{\text{WE}} = \text{High}$ . The read access time of 250ns makes the 2817 compatible with even high performance microprocessors (such as 8086-2) for zero wait state operation.

Writing to the 2817, however, is much easier than writing to either the 2716 EPROM or the 2816 E<sup>2</sup>PROM. Writing to a 2716 EPROM is accomplished by first erasing the EPROM completely with ultraviolet light. An EPROM is then programmed before being placed into its target system. When writing to a 2816 E<sup>2</sup>PROM, the chip is first erased in circuit by applying a high voltage exponential rise time programming pulse and placing logical 1's on the data bus. After erasure, the 2816 E<sup>2</sup>PROM is then programmed with another programming pulse.

By contrast, the 2817 is as simple as writing to a RAM:  $\overline{\text{CE}} = \overline{\text{WE}} = \text{LOW}$ ,  $\overline{\text{OE}} = \text{HIGH}$ . All the control signals initiating the write cycle are TTL level. Like a RAM, the user does not have to erase the memory location before writing to it; the erase-before-write is performed automatically by on-chip intelligence. The input addresses and data are latched by the  $\overline{\text{WE}}$  input. Latches make the 2817 E<sup>2</sup>PROM appear RAM-like to the user even though the programming time for an E<sup>2</sup>PROM cell is inherently slower than a RAM cell. The on-chip timer generates the internal programming pulse using the external timing capacitor. The  $\overline{\text{RDY}}/\overline{\text{BUSY}}$  output goes low to indicate that a write operation is in progress. The system CPU can then continue its normal processing work until the 2817's  $\overline{\text{RDY}}/\overline{\text{BUSY}}$  output goes back high, at which time another byte write or read operation can be initiated.

### SIMPLE INTERFACE REQUIREMENTS

The 2817 does not need the external timing and complex digital switching logic that is required for interfacing the 2816 to a microprocessor bus. From an external circuitry standpoint, all that is needed is a static  $V_{\text{PP}}$  21V supply and a write protection circuit. The 2817 requires a static 21V for both read cycles and write operations. It will be possible to read the 2817 with either 5V or 21V on  $V_{\text{PP}}$  on parts shipped after January 1983. The write protection circuit is needed to prevent data loss during  $V_{\text{CC}}$  power transitions. The TTL SSI devices that are normally used in systems to drive the  $\overline{\text{CE}}$  and  $\overline{\text{WE}}$  inputs are typically unstable when  $V_{\text{CC}}$  is below 4 volts. These TTL drivers could cause a spurious write operation to occur when  $V_{\text{CC}}$  is below normal operating level, and a data byte would be lost (see Figure 1). To prevent data loss under such conditions, the  $\overline{\text{WE}}$  input should be maintained at  $V_{\text{IH}}$  (or equal to  $V_{\text{CC}}$ ) during  $V_{\text{CC}}$  power transitions (see Figure 2).

# A WRITE PROTECTION CIRCUIT EXAMPLE

A circuit satisfying the condition of  $\overline{WE}$  at  $V_{IH}$  (or  $V_{CC}$ ) to prevent a spurious write operation is shown in Figure 3. The components used are all readily available, inexpensive, and occupy little board space. This circuit has been tested extensively at 25 °C.

The circuit operates by monitoring system  $V_{CC}$  and using it to qualify the system  $\overline{WE}$  output signal. The zener diode determines when transistor Q1 turns on and off.

When  $V_{CC}$  is below 4.5V the zener is not have sufficient voltage across it to remain on. When the zener is not conducting, Q1 is off. Q2 is then turned on, bringing the base of Q3 low. Q3 is turned off which causes the  $\overline{WE}$  input of the 2817 to be pulled to  $V_{CC}$ . In this condition the system  $\overline{WE}$  signal will not be able to affect the  $\overline{WE}$  input of the 2817. When  $V_{CC}$  is above 4.5V, Q1 is on, Q2 is off, and Q3 acts as an inverter, permitting the system  $\overline{WE}$  signal to pass through.

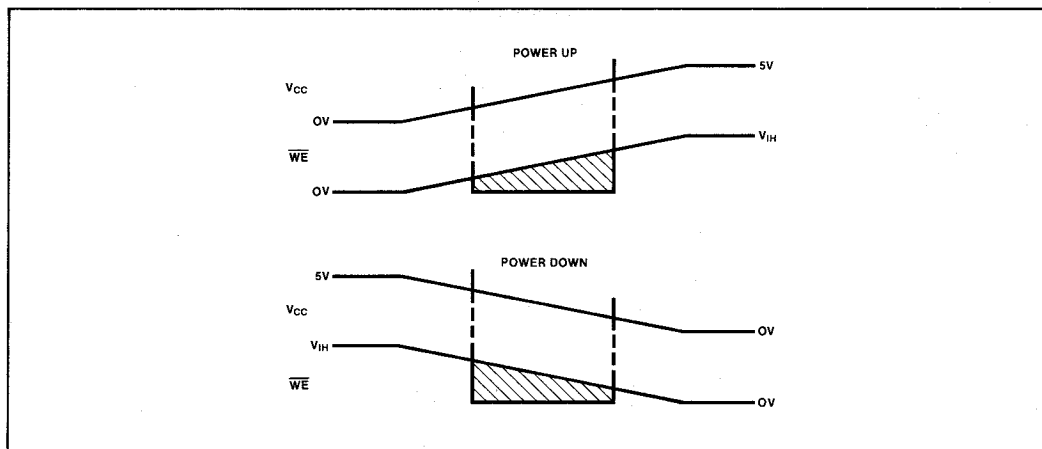


Figure 1. Typical TTL Driver Instability during  $V_{CC}$  Power Transitions

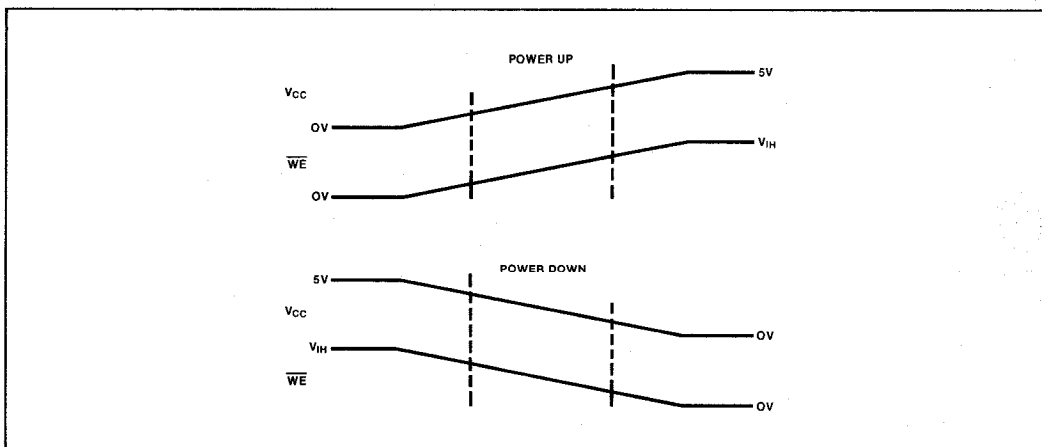


Figure 2. Controlled  $\overline{WE}$  during  $V_{CC}$  Power Transitions

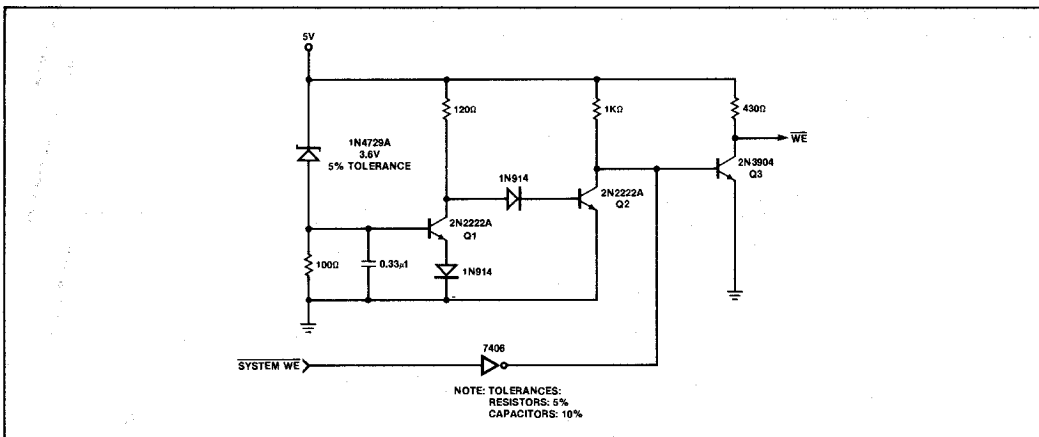


Figure 3. 2817 Write Protection Circuit

### ADVANTAGE OF STATIC 21V

With the 2817 the system designer can leave  $V_{PP}$  on during normal operation rather than switch  $V_{PP}$  on and off. The 2817 on-chip intelligence automatically generates and shapes the programming pulses internally from the external 21V static supply. The 2816 requires external logic to produce a switching  $V_{PP}$  signal to accomplish the same task. If the 2817's  $V_{PP}$  had to be switched on for write cycles there would be some delay involved in bringing  $V_{PP}$  up to 21V. There would also be noise coupled into the surrounding TTL circuitry resulting from the fast switching of a high voltage.

Since it is generally a good practice to decouple any power supply, it is recommended that  $V_{PP}$  (Pin 1) be decoupled with a 0.1 microfarad capacitor.

### 21V Is Easy To Obtain


The 21V for  $V_{PP}$  can come from a number of sources. A separate AC input 21V supply could be used. A less expensive alternative for a small array of 2817's is a DC to DC converter. Modular 5V to 21V (or 24V) converters are available from various power supply vendors that can provide anywhere from 30mA to 200mA. (See Appendix A) An example would be the ELPAC/TDK CE-0299: It costs from \$6 to \$14, can supply 3 2817's (1 device in write mode = 15mA, 2 devices in read or standby mode = 16mA), and fits into a 24 dip socket. (If a 28 pin socket is used instead of a 24 pin socket, the former could be used as an additional memory socket when the circuit is upgraded to the 5V-only 2817A.)

The TL497A-based circuit shown in the 2817 data sheet costs about \$4 in large quantities. It can provide enough current for 8 devices.

### LARGE ARRAYS

An array of 8 2817's will require only 71mA (15mA for one device in write mode, 56mA for 7 devices in standby or read mode).

The TL497A based circuit discussed above can be used. It will output 21V or 24V. There are also numerous 5V to 24V converters available at this current rating and higher. To provide a regulated 21V output from these converters an LM317 voltage regulator can be used as shown in Figure 4.

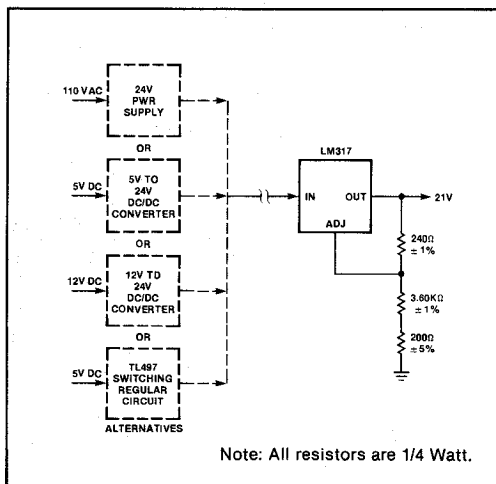Figure 4. Voltage Regulator For Supplying  $V_{PP}$  In Large Arrays

## CONNECTING THE RDY/BUSY OUTPUT TO THE SYSTEM

The 2817's on-chip intelligence controls the programming cycle and provides a system feedback signal. When the address and data are latched into the 2817 by the WE input pulse, the RDY/BUSY output goes low indicating that a write operation is in progress. After a predetermined amount of time has elapsed to insure successful programming, the RDY/BUSY output returns high to indicate the write operation is complete.

The system CPU can deal with the 2817 RDY/BUSY output in one of two ways: the output can be used as an interrupt to the CPU, or it can be polled.

If the CPU is not needed for system functions while the E<sup>2</sup>PROM write cycles are in progress, then polled mode would be acceptable since it usually requires less software and/or hardware than interrupt mode. Otherwise, an interrupt-driven mode should be used.

Figures 5, 6, and 7 show how the RDY/BUSY output could be used as an interrupt in 8088, 8085A, or 8051-based systems, respectively. Figures 8 and 9 show hardware diagrams for polled mode operation.

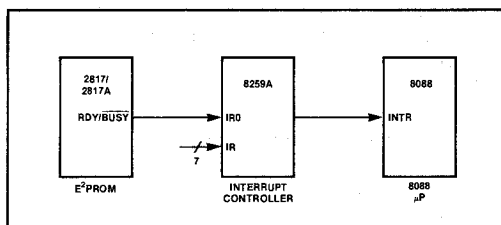


Figure 5. Interrupt-Driven 8088 System

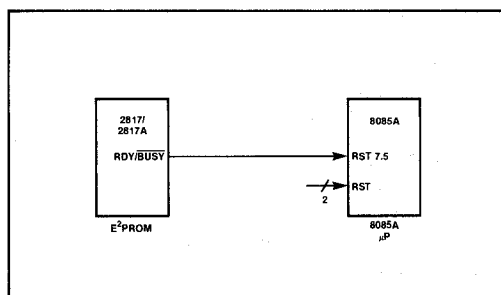


Figure 6. Interrupt-Driven 8085A System

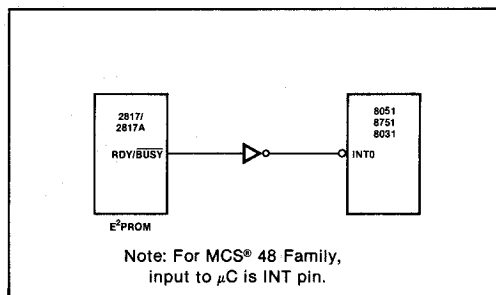


Figure 7. Interrupt-Driven Microcontroller System

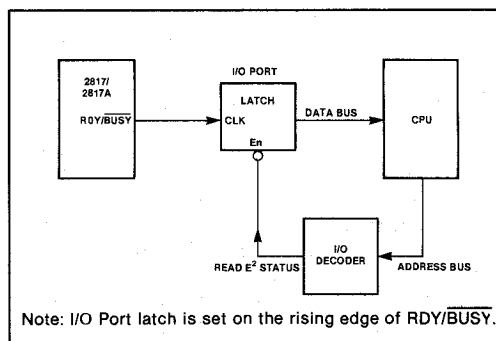


Figure 8. Polled Mode, General

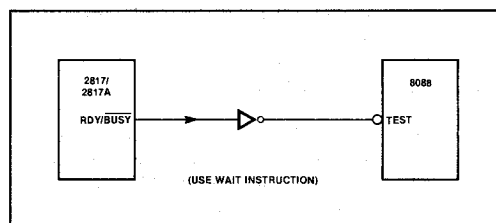


Figure 9. Polled Mode For 8088 System

Polled mode with the 8088 can be done easily and effectively with minimal software and hardware as shown in Figure 9. To write to the 2817, simply do the following:

```
MOV AL, DATA BYTE ;LOAD AL REG WITH DATA
MOV E²PROM, AL ;WRITE IT TO E2
WAIT ;WAIT UNTIL WRITE OPERATION
;IS DONE
```



The 8088 will remain in a wait state while the test input is high (RDY/BUSY is low). When the test input returns low, program execution will continue with the next instruction following 'WAIT'.

The following two steps describe how a data block can be transferred from RAM to E<sup>2</sup>PROM in an interrupt-driven system. The operation is initiated by two actions: (1) a software pointer is loaded indicating the target E<sup>2</sup>PROM data block (2) a system memory write cycle is initiated to the first address of the E<sup>2</sup>PROM data block. Normal processing then continues while an interrupt subroutine such as the one shown in Figure 10 does the rest.

As each E<sup>2</sup>PROM write operation is completed, the interrupt subroutine is called up via the RDY/BUSY output to write the next byte. When the data block has been completely transferred to E<sup>2</sup>PROM, a software flag is cleared to indicate the status to the CPU.

### FUTURE UPGRADABILITY TO THE 5V-ONLY 2817A

A powerful set of intelligence is currently integrated on to the 2817. In the future, the circuitry to generate the programming voltage from a 5 volt supply will be integrated on-chip with the 2817A. Figure 11 a) and b) shows how to design in a jumper and a resistor location for a 2817 PC board layout so that the 5V-only 2817A can be easily installed in the future. Table I shows the pinout differences between the two devices.

The 2817A has a write protection circuit on-chip so that the external circuit in Figure 3 is not required. This circuit can remain on board and be used with the 2817A if desired.

The RDY/BUSY pin of the 2817A is an open drain output. The design enables the user to tie the RDY/BUSY line from 2 or more 2817A's together. If two 2817A's are tied together, the RDY/BUSY line will not go back high until both 2817A's are successfully programmed. This is ideal in 16 bit bus architectures. The 7.5K resistor shown is a minimum value for 1 TTL load, since the total sink current should not exceed the device rating: 2.1mA @ VOL = 0.4V.

The resistor value can be calculated as follows:

$$R_{(PULLUP)} = \frac{4.6V}{2.1 \text{ MA} - I_{IL}}$$

Where I<sub>IL</sub> = The total V<sub>IL</sub> input current of all devices connected to RDY/BUSY.


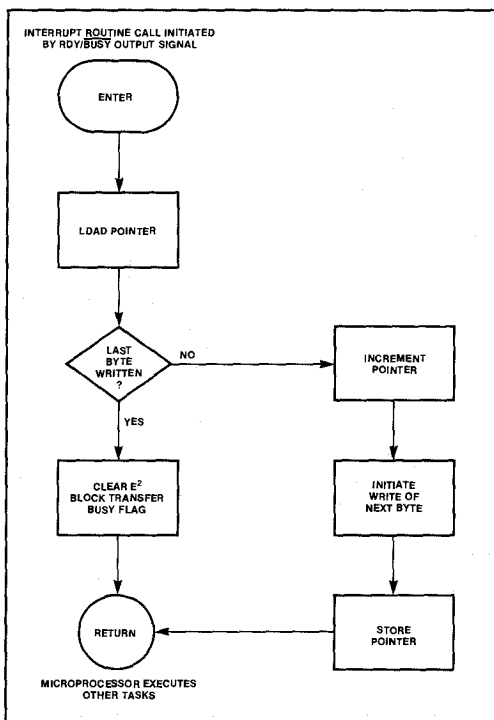



Figure 10. Interrupt Subroutine Servicing Blocks Transfer To 2817

Table 1.  
Differences in Pinout of 2817 and 2817A

Device	PINS		
	1	2	26
2817	VPP	RDY/ <u>BUSY</u>	TIMING CAP
2817A	RDY/ <u>BUSY</u>	NC	NC

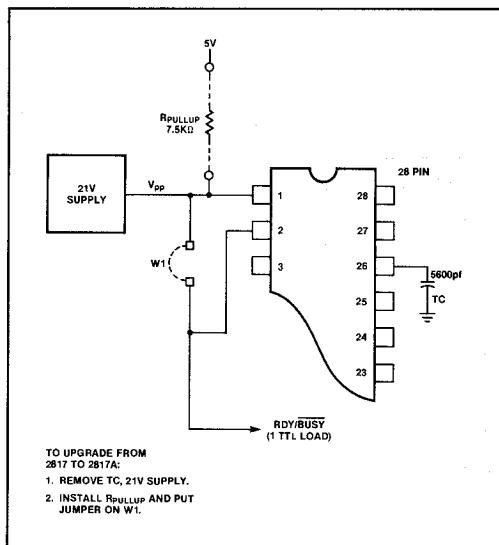

**Figure 11A. Upgrade Layout For 2817/2817A**

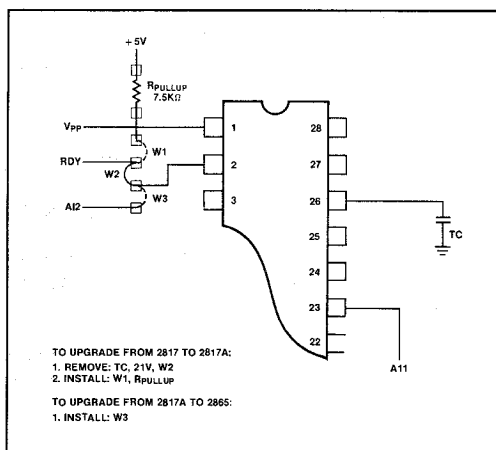

**Figure 11B. Upgrade Layout For 2817/2817A/2865**

THIS IS A FEW OF THE MANY 5V TO 21V (OR 24V) CONVERTERS THAT ARE AVAILABLE.				
DESCRIPTION	V <sub>OUT</sub>	I <sub>OUT</sub>	EST. COST (1)	SIZE
ELPAC/TDK CE-0299	21V	35 MA	\$ 6 (14)	24 PIN DIP
DATel UPM-24/40-D5	24V	40 MA	\$29 (46)	2.5 SQ IN
RELIABILITY, INC. VA12-12	23V	40 MA	\$17 (24)	24 PIN DIP
INTRONICS DCR 5/12-12	24V	80 MA	\$36 (40)	24 PIN DIP

NOTES: 1. The numbers in the 'cost' column indicated both large and small quantities as follows: Large Qty's (small qty's).

## VENDOR INFORMATION

VENDOR	ADDRESS	PHONE NUMBER
ELPAC/TKD POWER SYSTEM	3131 S. STANDARD AVE. SANTA ANA, CA 92705	(714) 979-4440
DATEL/INTERSIL	11 CABOT BLVD. MANSFIELD, MA. 02048	(617) 339-9341 (617) 828-8000
RELIABILITY, INC. OF TEXAS	P.O. BOX 218370 HOUSTON, TEXAS 77218	(713) 492-0550
INTRONICS	NEWTON, MASS.	(617) 964-4000

## ALABAMA

Intel Corp.  
303 Williams Avenue, S.W.  
Suite 1422  
Huntsville 35801  
Tel: (205) 533-9353

## ARIZONA

Intel Corp.  
10210 N. 25th Avenue,  
Suite 11  
Phoenix 85021  
Tel: (602) 889-4980

## CALIFORNIA

Intel Corp.  
1010 Hurley Way  
Suite 300  
Sacramento 95825  
Tel: (916) 929-4078

Intel Corp.  
7670 Opportunity Road  
Suite 135  
San Diego 92111  
Tel: (714) 268-3553

Intel Corp.  
2000 East 4th Street  
Suite 100  
Santa Ana 92705  
Tel: (714) 835-9642  
TWX: 910-595-1114

Intel Corp.  
3375 Scott Boulevard  
Santa Clara 95051  
Tel: (408) 987-8086  
TWX: 910-539-9279

Intel Corp.  
5530 Corbin Avenue  
Suite 120  
Torrance 91356  
Tel: (213) 708-0333  
TWX: 910-495-2045

## COLORADO

Intel Corp.  
4445 Northpark Drive  
Suite 100  
Colorado Springs 80907  
Tel: (303) 594-6622

Intel Corp.  
650 S. Cherry Street  
Suite 720  
Denver 80222  
Tel: (303) 321-8086  
TWX: 910-831-2289

## CONNECTICUT

Intel Corp.  
36 Padanaram Road  
Danbury 06810  
Tel: (203) 792-8366  
TWX: 710-456-1199

EMC Corp.  
48 Purnell Place  
Manchester 06040  
Tel: (203) 646-8085

EMC Corp.  
393 Center Street  
Wallingford 06492  
Tel: (203) 265-6991

## FLORIDA

Intel Corp.  
1500 N.W. 62nd Street  
Suite 104  
Ft. Lauderdale 33309  
Tel: (305) 771-0600  
TWX: 510-856-9407

Intel Corp.  
500 N. Maitland  
Suite 205  
Maitland 32751  
Tel: (305) 628-2393  
TWX: 810-853-9219

## GEORGIA

Intel Corp.  
3300 Holcomb Bridge Road  
Suite 225  
Norcross 30092  
Tel: (404) 449-0541

## ILLINOIS

Intel Corp.  
2550 Golf Road,  
Suite 815  
Rolling Meadows 60008  
Tel: (312) 981-7200  
TWX: 910-651-5881

## INDIANA

Intel Corp.  
9100 Purdue Road  
Suite 400  
Indianapolis 46268  
Tel: (317) 875-0623

## IOWA

Intel Corp.  
St. Andrews Building  
1930 St. Andrews Drive N.E.  
Cedar Rapids 52402  
Tel: (319) 393-5510

## KANSAS

Intel Corp.  
8400 W. 110th Street  
Suite 170  
Overland Park 66210  
Tel: (913) 642-8080

## LOUISIANA

Industrial Digital Systems Corp.  
2332 Severn Avenue  
Suite 202  
Metairie, LA 70001  
Tel: (504) 831-8492

## MARYLAND

Intel Corp.  
7257 Parkway Drive  
Hanover 21076  
Tel: (301) 796-7500  
TWX: 710-862-1944

Intel Corp.  
1820 Elton Road  
Silver Spring 20903  
Tel: (301) 431-1200

## MASSACHUSETTS

Intel Corp.  
27 Industrial Avenue  
Chelmsford 01824  
Tel: (617) 256-1800  
TWX: 710-343-6333

EMC Corp.  
381 Elliot Street  
Newton 02164  
Tel: (617) 244-4740  
TWX: 922531

## MICHIGAN

Intel Corp.  
25500 Northwestern Hwy.  
Suite 401  
Southfield 48075  
Tel: (313) 353-0920  
TWX: 810-244-4915

## MINNESOTA

Intel Corp.  
3500 W. 80th Street  
Suite 360  
Bloomington 55431  
Tel: (612) 835-6722  
TWX: 910-576-2867

## MISSOURI

Intel Corp.  
4203 Earth City Expressway  
Suite 131  
Earth City 63045  
Tel: (314) 291-1990

## NEW JERSEY

Intel Corp.  
3300 Plaza III  
Raritan Center  
Edison 08837  
Tel: (201) 225-3000  
TWX: 710-480-6238

## NEW MEXICO

BFA Corp.  
P.O. Box 1237  
Las Cruces 88001  
Tel: (505) 523-0601  
TWX: 910-953-0543  
BFA Corp.  
3705 Westfield, N.E.  
Albuquerque 87111  
Tel: (505) 292-1212  
TWX: 910-989-1157

## NEW YORK

Intel Corp.  
300 Motor Parkway  
Hauppauge 11787  
Tel: (516) 231-3300  
TWX: 510-227-6236  
Intel Corp.  
80 Washington Street  
Poughkeepsie 12601  
Tel: (914) 473-2303  
TWX: 510-248-0060

Intel Corp.  
211 White Spruce Boulevard  
Rochester 14623  
Tel: (716) 424-1050  
TWX: 510-253-7391

T-Squared  
4054 Newcourt Avenue  
Syracuse 13206  
Tel: (315) 463-8592  
TWX: 710-541-0554

T-Squared  
7353 Pittsford  
Victor Road  
Victor 14564  
Tel: (716) 924-9101  
TWX: 510-254-8542

## NORTH CAROLINA

Intel Corp.  
2306 W. Meadowview Road  
Suite 206  
Greensboro 27407  
Tel: (919) 294-1541

## OHIO

Intel Corp.  
6500 Poe Avenue  
Dayton 45414  
Tel: (513) 880-5350  
TWX: 810-450-2528

Intel Corp.  
Chagrin-Brainard Bldg., No. 300  
28001 Chagrin Boulevard  
Cleveland 44122  
Tel: (216) 464-2736  
TWX: 810-427-9298

## OKLAHOMA

Intel Corp.  
4157 S. Harvard Avenue  
Suite 123  
Tulsa 74101  
Tel: (918) 749-8668

## OREGON

Intel Corp.  
10700 S.W. Beaverton  
Hillsdale Highway  
Suite 324  
Beaverton 97005  
Tel: (503) 641-8086  
TWX: 910-467-8741

## PENNSYLVANIA

Intel Corp.  
510 Pennsylvania Avenue  
Fort Washington 19034  
Tel: (215) 641-1000  
TWX: 510-661-2077  
Intel Corp.  
201 Penn Center Boulevard  
Suite 301W  
Pittsburgh 15235  
Tel: (412) 823-4970  
Q.E.D. Electronics  
300 N. York Road  
Hattboro 19040  
Tel: (215) 674-9600

## TEXAS

Intel Corp.  
12300 Ford Road  
Suite 380  
Dallas 75234  
Tel: (214) 241-0887  
TWX: 910-860-5617  
Intel Corp.  
7322 S.W. Freeway  
Suite 1490  
Houston 77074  
Tel: (713) 988-8086  
TWX: 910-881-2490  
Industrial Digital Systems Corp.  
5925 Sovereign  
Suite 101  
Houston 77036  
Tel: (713) 988-9421  
Intel Corp.  
313 E. Anderson Lane  
Suite 314  
Austin 78752  
Tel: (512) 454-3628

## UTAH

Intel Corp.  
268 West 400 South  
Salt Lake City 84101  
Tel: (801) 533-8086

## VIRGINIA

Intel Corp.  
1501 Santa Rosa Road  
Suite C-7  
Richmond 23288  
Tel: (804) 282-5668

## WASHINGTON

Intel Corp.  
110 110th Avenue N.E.  
Suite 510  
Bellevue 98005  
Tel: (206) 453-8086  
TWX: 910-443-3002

## WISCONSIN

Intel Corp.  
150 S. Sunnyslope Road  
Brookfield 53005  
Tel: (414) 784-9080



INTEL CORPORATION, 3065 Bowers Avenue, Santa Clara, CA 95051 (408) 987-8080

Printed in U.S.A./G-527/1282/5K/JR/JS